

# Chapter

3

## Simplification OF Boolean Functions.

### # The Map Method

#### ① Two variable Map

$x$	$y$	$\bar{x}$	$\bar{y}$	$\rightarrow 0 = x$	binary	Gray
0	0	1	1	$\rightarrow 0 = x$	00	00
1	0	0	1	$\rightarrow 1 = y$	01	01
0	1	1	0	$\rightarrow 1 = y$	10	10
1	1	0	0	$\rightarrow 1 = x$	11	11

↓      ↓

$m_0$	$m_1$	$m_2$	$m_3$
$m_0$	$m_3$	$m_2$	$m_1$

000      000  
001      001  
010      011  
011      010

#### ② Three variable Map

$m_0$	$m_1$	$m_2$	$m_3$
$m_0$	$m_3$	$m_2$	$m_1$

JK  
Karnaugh map  
Max term minterm & function to  
Min term minterm & complement form  
Date \_\_\_\_\_  
Page \_\_\_\_\_

$y_2 \rightarrow$

$\bar{x}_2$	$\bar{y}_2$	$y_2$	$\bar{y}_2$
0	0	1	0
0	1	0	1
1	0	1	0
1	1	0	1

(ii) Four Variable Mdp

$y_2 \rightarrow$

$\bar{x}_2$	$\bar{y}_2$	$y_2$	$\bar{y}_2$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

$\bar{x}_2$	$\bar{y}_2$	$y_2$	$\bar{y}_2$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

we can make a pair of adjacent 1's in a pair of

to accommodate numbers of 1's in a pair of

76, 8, 14, 2

In this case we have 2 pairs as follows:

$wx$	$xy$	$yz$	$w\bar{x}\bar{y}\bar{z}$
11	11	11	0000
11	11	00	0100
11	00	11	1000
00	11	11	1001

1st pair:  
 $w\bar{x}\bar{y}\bar{z}$

2nd pair:  
 $\bar{x}y$

Hence the simplified function is

$$F = w\bar{x} + \bar{x}y$$

Min term  $\square$  a  
Max term  $\square$  a

Normal Complement  
Complement  
Sop

Date \_\_\_\_\_  
Page \_\_\_\_\_

⑪  $F = \bar{x}y_2 + y_1\bar{z} + \bar{x}y_2 + x\bar{y}_2$

Soln:

Since there are variables, we need to draw a k-Mdp.

$y_2$	$\bar{y}_2$	$y_2$	$\bar{y}_2$
$\bar{y}_2$	$y_2$	$\bar{y}_2$	$y_2$
0	1	1	0
x	0	0	1

$y_2$	$\bar{y}_2$	$y_2$	$\bar{y}_2$
$\bar{y}_2$	$y_2$	$\bar{y}_2$	$y_2$
1	0	0	1
x	1	1	0

In min terms,

Here, we can make a pair of adjacent 1's trying to accommodate the numbers of 1's in pairs of F  $16, 8, 4, 2$ .

In this case we have 2 pairs as follows,

1st pair:  $y_2$   
2nd pair:  $x\bar{z}$

Hence simplified Function is

$$SOP = F = y_2 + x\bar{z}$$

In max terms,

Here, we made a pair of adjacent 0's trying to accommodate the number of 0's in pair of  $16, 8, 4, 2$ .

$\bar{w}x$	$w\bar{x}$	$\bar{y}z$	$y\bar{z}$	$\bar{w}\bar{y}$	$w\bar{y}$	$\bar{x}z$	$x\bar{z}$
1	0	1	0	1	0	1	0
0	1	0	1	0	1	0	1
w	x	y	z	w	x	y	z

POS =  $(y_2 + \bar{x}) \cdot (x + z)$

⑫

$$F(A, B, C, D) = \sum(0, 1, 2, 3, 5, 8, 9, 10)$$

Simply it in POS and SOP.

$\bar{w}\bar{x}$	$w\bar{x}$	$\bar{y}z$	$y\bar{z}$	$\bar{w}\bar{y}$	$w\bar{y}$	$\bar{x}z$	$x\bar{z}$
0	0	0	1	1	0	1	0
0	1	1	0	0	1	0	1
w	x	y	z	w	x	y	z

$(x\bar{w}\bar{y})(\bar{x}\bar{z})$

$$\begin{aligned} F &= xy + x\bar{z} + y\bar{z} + \bar{z} \cdot 2 \\ &= xy(2 + \bar{z}) + x\bar{z} + y\bar{z} \\ &= xy(2 + \bar{z}) + x\bar{z} + y\bar{z} \\ &= y_2(x + \bar{z}) + \bar{y}_2(y + \bar{z}) \\ &= y_2 + x\bar{z} \end{aligned}$$

$$F = (y_2 + \bar{x}) \cdot (x + z)$$

In this case we have 2 pairs as follows,

# Pos

product of sum

(max term ma hunx)

# Sop

sum of product

(min term ma hunx)

Solved:

$$pos = (x+y)(x+z)$$

$$sop = x + yz$$

Converting it into Standard Form:

$$sop = x + yz$$

$$= (xy + \bar{y}z) + yz(x + \bar{x})$$

$$= xy + x\bar{y} + xyz + \bar{x}yz$$

$$= xy\bar{z} + xy\bar{z} + x\bar{y}z + x\bar{y}\bar{z} + xyz + \bar{x}yz$$

0-complement

$$111 \quad 110 \quad 101 \quad 100 \quad 111 \quad 011$$

$$= \Sigma(3, 4, 5, 6, 7)$$

not pos  $pos = (x+y)(x+z)$

$$= (xy + \bar{y}z)(x + z + y\bar{z})$$

$$= (xy + \bar{y}z)(x + y + z)(x + \bar{y} + z)$$

$$= 000 \quad 001 \quad 000 \quad 010$$

$$= \Pi(0, 1, 2)$$

Complement:

$$pos = (x+y)(x+z)$$

$$\bar{F} = (\bar{x} + \bar{y}) \cdot (\bar{x} + \bar{z})$$

- using demorgan law

$$= \bar{x}(\bar{y} + \bar{z})$$

$$sop = (x + yz)$$

$$F = \bar{x} + \bar{y}z$$

- using demorgan law

$$= \bar{x}\bar{y} + \bar{x}\bar{z}$$

① Simplify the following function using K-map.

$$F = \Sigma(3, 4, 5, 6, 7)$$

$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	$yz$	
00	01	11	10	
$\bar{x}$	0	1	1	0
x	1	1	0	1

① simplified in sop

we make pair of 1,

② simplified in pos

we make pair of 0,

$$F = x + yz$$

$$F = \bar{x}(\bar{y} + \bar{z})$$

③ complement in sop

we make pair of 0,

$$F = \bar{x}\bar{y} + \bar{x}\bar{z}$$

④ complement in pos

we make pair of 1,

$$F = (x+y)(x+z)$$

~~Clear~~

Date \_\_\_\_\_  
Page \_\_\_\_\_

Date March 27  
Page Tuesday

②

$$F = \Sigma (0, 1, 2, 4, 5, 6)$$

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	$yz$
$\bar{x}$	00	01	11	10
$x$	11	10	01	00

① Simplified in SOP

Here we make pair  
of 1.

In this case we have  
2 pairs.

$$F = \bar{z} + x\bar{y}$$
 [Normal]

② Simplified in POS

Here we make pair of  
1.

In this case we have  
2 pairs.

$$F = z(\bar{x} + y)$$
 [Complement]

① Complement in SOP

Here we make pair of 0.  
In this case we have 2  
pairs.

$$F = yz + \bar{x}z$$
 [Complement]

② Simplified in POS

Here we make pair of 0.  
In this case we have  
2 pairs.

$$F = (x + \bar{z})(y + \bar{z})$$

Normal

## # Don't Care Conditions

① Simplify using don't care conditions.

$$F = \Sigma (0, 1, 2, 4, 5, 6, 8, 10)$$

$$d = \Sigma (7, 14, 13)$$

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{C}\bar{D}$	00	01	11	10
$\bar{C}D$	10	11	X	11
$C\bar{D}$			X	X
$CD$			11	X

$$F = C\bar{D} + \bar{A}BD + \bar{B}\bar{D}$$

$$F(w, x, y, z) = \Sigma (7, 13, 7, 11, 13)$$

$$d = \Sigma (10, 2, 3)$$

	$\bar{w}\bar{z}$	$\bar{w}z$	$w\bar{z}$	$wz$
$\bar{w}\bar{z}$	00	1X	1	1X
$\bar{w}z$	01	0	X	1
$w\bar{z}$	11	0	0	1
$wz$	10	0	0	1

① Simplified in SOP

$$F = \bar{w}\bar{x} + yz$$

[Normal]

② Simplified in POS

$$F = (\bar{y} + \bar{z})(w + x)$$

[Complement]

③ Complement in SOP

$$F = \bar{z} + w\bar{y}$$

[Complement]

④ Complement in POS

$$F = z(\bar{w} + y)$$

[Normal]

SOP ko normal ma jni Auxa  $\rightarrow$  POS  
ma lagidihne tyo POS ko complement huy

i.e. SOP Normal  $\rightarrow$  POS to Complement

SOP Complement  $\rightarrow$  POS to normal

Date \_\_\_\_\_  
Page \_\_\_\_\_  
May 24  
Tuesday

## H. Five Variables Map [Eg]

		$CDE$	$\bar{C}\bar{D}\bar{E}$	$\bar{C}\bar{D}F$	$\bar{C}D\bar{E}$	$\bar{C}DF$	$C\bar{D}\bar{E}$	$C\bar{D}F$	$CD\bar{E}$	$CD\bar{F}$	$CDE$
		AB	000	001	011	010	110	111	101	100	111
		$\bar{A}\bar{B}$	00	0	1	3	2	6	7	5	4
		$\bar{A}B$	01	8	9	77	70	74	73	78	72
		AB	11	24	25	27	26	30	31	29	28
		$A\bar{B}$	10	76	77	79	78	82	83	81	80

$\leftarrow 0 \text{ to plane} \rightarrow$        $\leftarrow 1 \text{ to plane} \rightarrow$

Date \_\_\_\_\_  
Page \_\_\_\_\_

Date \_\_\_\_\_  
Page \_\_\_\_\_


(a) Simplify the Boolean Function:

$$F(1, B, 1, \vartheta, F) = \{1, 2, 4, 6, 9, 17, 18, 15, 19, 27, \\ 23, 27, 29, 31\}$$

	$\text{C}\bar{\text{D}}\text{E}$	$\bar{\text{C}}\text{D}\text{E}$	$\bar{\text{C}}\text{D}\bar{\text{E}}$	$\bar{\text{C}}\bar{\text{D}}\bar{\text{E}}$	$\text{C}\bar{\text{D}}\bar{\text{E}}$	$\text{C}\text{D}\bar{\text{E}}$	$\text{C}\text{D}\text{E}$	$\bar{\text{C}}\text{D}\bar{\text{E}}$
$\text{AB}$	$\text{C}\bar{\text{D}}\bar{\text{E}}$	$\bar{\text{C}}\bar{\text{D}}\bar{\text{E}}$	$\bar{\text{C}}\text{D}\bar{\text{E}}$	$\text{C}\bar{\text{D}}\text{E}$	$\text{C}\text{D}\bar{\text{E}}$	$\text{C}\text{D}\text{E}$	$\bar{\text{C}}\text{D}\text{E}$	$\bar{\text{C}}\bar{\text{D}}\bar{\text{E}}$
$\bar{\text{A}}\text{B}$	00	11	11	11	11	11	11	11
$\bar{\text{A}}\text{B}$	01	11	11	11	11	11	11	11
$\bar{\text{A}}\text{B}$	11	11	11	11	11	11	11	11
$\bar{\text{A}}\text{B}$	10	11	11	11	11	11	11	11

$$F = BE + \bar{A}\bar{B}\bar{E} + A\bar{D}F$$
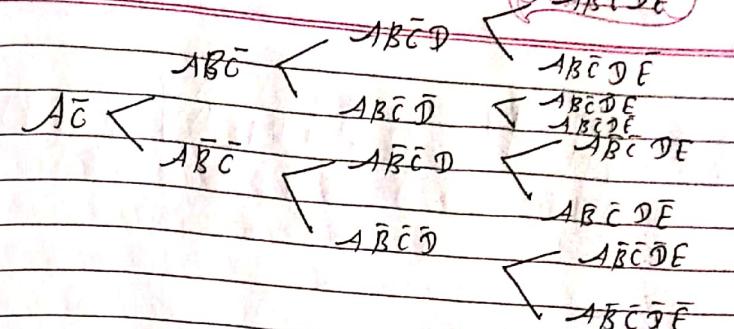
$$b) F = A\bar{C} + ACE + A\bar{C}\bar{E} + \bar{A}(CD) + \bar{A}\bar{D}F$$



$$F = A + C\bar{D} + \bar{D}\bar{E} \quad //$$

$$F = \bar{A}\bar{B} + A\bar{B}C + \bar{A}BD + AB\bar{E} + \bar{A}BE + \bar{A}D$$

	$\bar{C}\bar{D}\bar{E}$	$\bar{C}\bar{D}F$	$\bar{C}DF$	$\bar{C}\bar{F}\bar{E}$	$C\bar{D}\bar{E}$	$CD\bar{F}$	$C\bar{D}E$	$C\bar{D}\bar{E}$
$AB$	$CDE$	$\bar{C}\bar{D}E$	$\bar{C}DE$	$\bar{C}\bar{D}\bar{F}$	$C\bar{D}\bar{E}$	$CD\bar{F}$	$C\bar{D}E$	$C\bar{D}\bar{E}$
	$000$	$001$	$011$	$0100$	$110$	$111$	$101$	$100$
$AB$	$00$			$1$	$1$	$1$	$1$	
$\bar{A}B$				$1$	$1$	$1$	$1$	
$01$	$1$			$1$	$1$	$1$	$1$	$1$
$\bar{A}B$				$1$	$1$	$1$	$1$	
$11$	$1$			$1$	$1$	$1$	$1$	$1$
$AB$				$1$	$1$	$1$	$1$	
$10$	$1$	$1$	$1$	$1$	$1$	$1$	$1$	$1$
$\bar{A}B$				$1$	$1$	$1$	$1$	

$$F = AB + \bar{A}D + BE \quad //$$

① Simplify the Boolean Function:

$$F(A, B, C, D, E) = \{0_{12}, 4_{16}, 9_{17}, 13_{18}, 15_{19}, 17_{20}, \\ 23_{27}, 29_{29}, 31\}$$

	$CDE$	$\bar{C}DE$	$\bar{C}\bar{D}E$	$C\bar{D}E$	$CDE$	$\bar{C}\bar{D}\bar{E}$
$AB$	000	001	011	010	110	111
$\bar{A}\bar{B}$	00	11	11	11	11	11
$A\bar{B}$	11	11	11	11	11	11
$\bar{A}B$	10	11	11	11	11	11


$$F = BE + \bar{A}\bar{B}\bar{E} + A\bar{D}F$$

b)

$$F = A\bar{C} + ACE + AC\bar{E} + \bar{A}C\bar{D} + \bar{A}\bar{D}F$$

	$CE$	$\bar{C}E$	$\bar{C}\bar{E}$	$\bar{C}\bar{D}E$	$C\bar{D}E$	$CDE$	$\bar{C}\bar{D}\bar{E}$
$AB$	000	001	011	010	110	111	101
$\bar{A}\bar{B}$	00	11	11	11	11	11	11
$01$	1						
$A\bar{B}$							
$11$	1	1	1	1	1	1	1
$\bar{A}B$	1	1	1	1	1	1	1
$10$	1	1	1	1	1	1	1
$\bar{A}\bar{B}$	1	1	1	1	1	1	1

Date \_\_\_\_\_  
Page \_\_\_\_\_

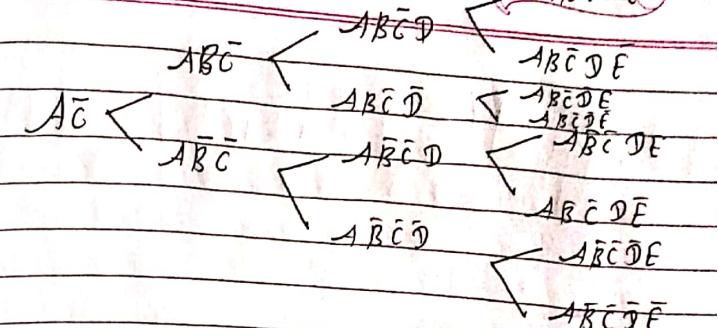

$$F = A + C\bar{D} + D\bar{F} //$$

c)

$$F = A\bar{B} + A\bar{B}C + \bar{A}BD + AB\bar{E} + \bar{A}B\bar{E} + A\bar{D}$$

	$C\bar{E}$	$\bar{C}\bar{E}$	$\bar{C}DE$	$\bar{C}\bar{D}E$	$C\bar{D}\bar{E}$	$CDE$	$\bar{C}\bar{D}\bar{E}$
$AB$	000	001	011	010	110	111	101
$\bar{A}\bar{B}$	00						
01	1						
$\bar{A}B$							
11	1						
$A\bar{B}$							
10	1	1	1	1	1	1	1
$\bar{A}\bar{B}$	1	1	1	1	1	1	1

$$F = A\bar{B} + \bar{A}D + BE //$$

# Chapter

4

## Combinational Logic

Design Procedure of Combinational Circuit:

- 1) The Problem is Stated.
- 2) The number of available input variables and required output variables is determined.
- 3) The input and output variables are assign letter or symbol.
- 4) The truthtable that defines the required relationships between inputs and outputs is derived.
- 5) The simplified boolean function for each output is obtained.
- 6) The logic diagram is draw.

Address:

- ↳ Design of a half adder circuit.
  - ↳ No. of input = 2 and output = 2.
  - ↳ Let 2 inputs be  $(x_1, x_2)$  and outputs be  $(S, C)$  where  $S$  is sum and  $C$  is carry.
  - ↳ Truth table of half adder.

Inputs		outputs	
x	y	s	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- ↳ From the truth table, we can generate the boolean Function as well.

$$S = \bar{x}y + \bar{y}x \quad ] \quad \text{Sop. Form}$$

$$= x \oplus y$$

$$C = xy \quad [C \text{ and } T \text{ have }]$$

- $$\rightarrow x \quad S = x \oplus y$$

fig: circuit diagram of half adder.

## Design of a Full adder circuit.

- 1) No. of input = 3 and output = 2.

- Let 3 inputs be  $(x, y, z)$  and outputs be  $(s, c)$ , where  $s$  is sum and  $c$  is carry.

Truth table of Full adders :

Inputs			Outputs	
x	y	z	s	c
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- ↳ From the truth table, we can generate boolean equation:

$$\begin{aligned}
 S &= \bar{x}\bar{y}z + \bar{x}y\bar{z} + \bar{x}\bar{y}\bar{z} + xy\bar{z} \\
 &= \bar{x}(\bar{y}z + y\bar{z}) + \bar{x}(\bar{y}\bar{z} + yz) \\
 &= \bar{x}(x \oplus z) + x(y \odot z) \\
 &= \bar{x}(\overline{y \oplus z}) + x(y \odot z) \\
 &= (\bar{x} \odot (\bar{y} \oplus z)) + x(\bar{y} \oplus z)
 \end{aligned}$$

7 bit kō xor & w XOR

Some fun x.

$$\begin{aligned}
 C &= \bar{x}yz + x\bar{y}z + xy\bar{z} + xyz \\
 &= z(\bar{x}y + x\bar{y}) + xy(\bar{z} + z) \\
 &= z(x \oplus y) + xy
 \end{aligned}$$

$$y_2(\bar{x}+x) + x(\bar{y}_2+y_2)$$

$$x(y \oplus z) + y_2$$

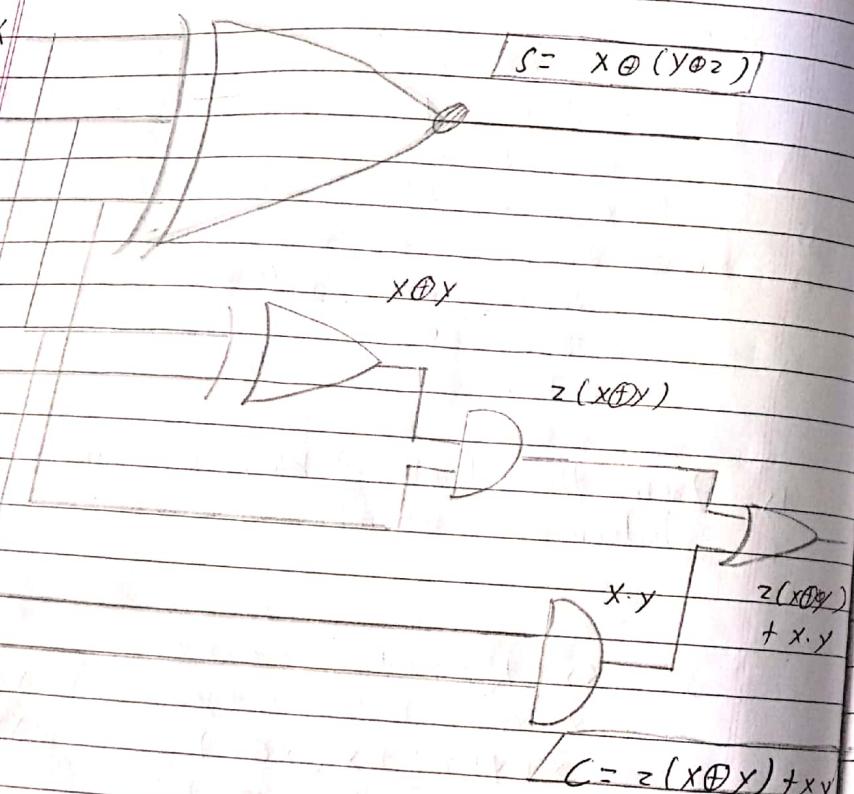


Fig: Circuit diagram of Full adders

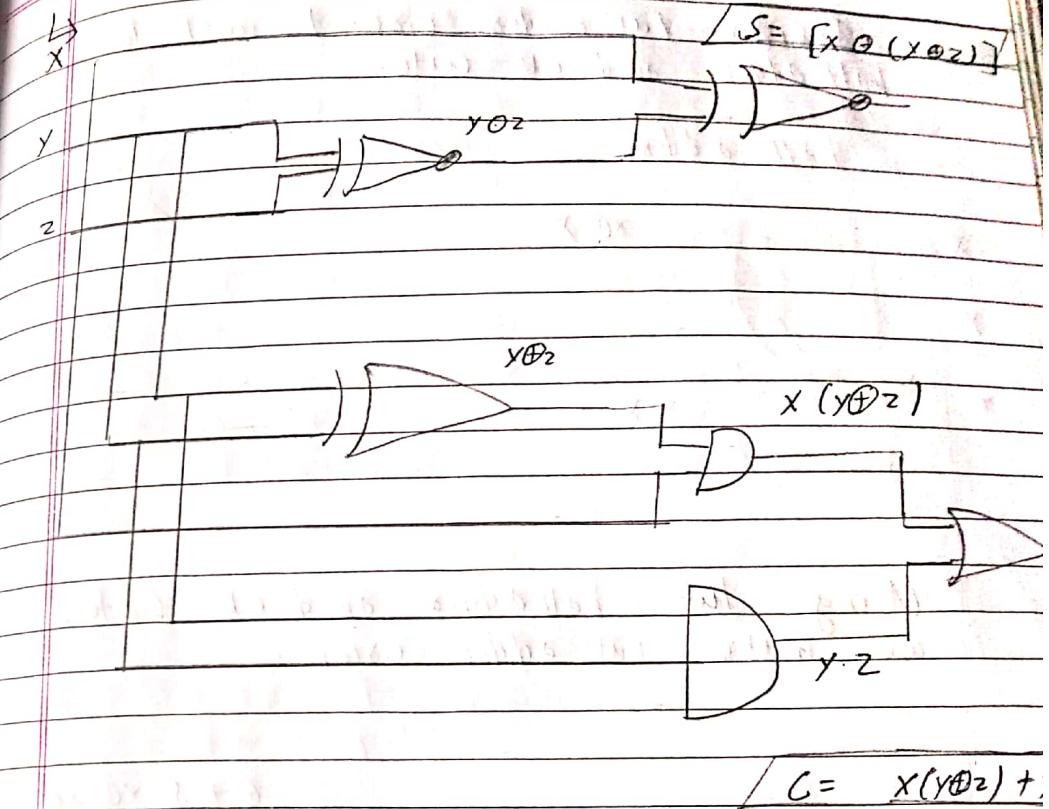



Fig: Circuit diagram of Full adders

[optional]


# Code Conversion Circuit

Design Full adder circuit with two half adder and OR Gate.

half adder:

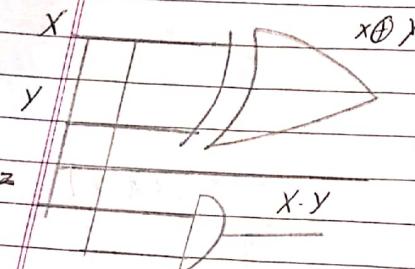

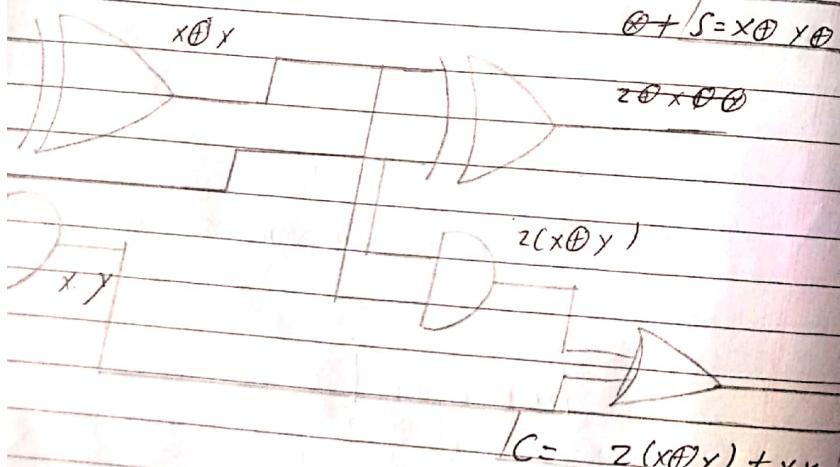Using two half adder and OR Gate, we make full adder circuit.



Logic diagram of BCD to excess 3 converter.

design of BCD to excess 3 converter.

No. of inputs = 4 and output = 4

Let inputs be A, B, C, D and outputs be w, x, y, z.

Truth table:

Inputs				Outputs			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	2
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	1	1	0	0
1	1	0	0	1	1	0	0

Boolean expression using k-map:

for w,  $\bar{C} \bar{D}$ ,  $\bar{C} D$ ,  $C \bar{D}$

$\bar{A} \bar{B}$		$\bar{C} \bar{D}$	$\bar{C} D$	$C \bar{D}$
$\bar{A} B$		1	1	1
$A \bar{B}$	x	x	x	x
$A B$	1	1	x	x

$$\begin{aligned}
 W &= A + B \bar{C} + B D \\
 &= A + \cancel{B} (\bar{C} + D) \\
 &= A + B (C + D)
 \end{aligned}$$

For  $x$ ,

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{A}\bar{B}$	1	1	1	1
$\bar{A}B$	1			
$A\bar{B}$	X	X	X	X
$AB$	1	X	X	X

For  $y$ ,

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{A}\bar{B}$	1			
$\bar{A}B$	1	1		
$A\bar{B}$		X	X	X
$AB$		1	X	X

$$\begin{aligned} X &= A\bar{D} + \bar{B}C + \bar{B}\bar{D} + BC\bar{D} \\ &= \bar{B}(C+\bar{D}) + B\bar{C}\bar{D} \\ &= C\bar{D} \end{aligned}$$

For  $z$ ,

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{A}\bar{B}$	1	1	1	1
$\bar{A}B$	1			
$A\bar{B}$	Y	Y	X	Y
$AB$	1	-	Y	Y

$$Z = \bar{D}$$

$$\begin{aligned} X &= \bar{B}(C+\bar{D}) + B(C\bar{D}) \\ &= B\oplus(C+\bar{D}) \end{aligned}$$

Date \_\_\_\_\_  
Page \_\_\_\_\_

Date \_\_\_\_\_  
Page \_\_\_\_\_

A

B

C

D

B.C.

B.D

(C+D)

B

$$w = A+B+C+BD$$

$$x = B\oplus(C+\bar{D})$$

$$y = (C\oplus D)$$

$\bar{D}$

$Z = \bar{D}$

Fig: Logical diagram of binary to excess 3 converter.

## Q# Binary to Gray Code converter (8 bit)

↳ design of logical circuit that converts 3 bit binary to 3 bit grey code.

↳ let input be  $x, y, z = 3$  and output be  $A, B, C = 3$ .

↳ Truth table.

Inputs			Outputs		
$x$	$y$	$z$	$A$	$B$	$C$
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	0	0

Boolean expression:

For  $A$ ,

$$\begin{aligned}
 A &= x\bar{y}\bar{z} + x\bar{y}z + xy\bar{z} + xyz \\
 &= x\bar{y}(\bar{z} + z) + xyz(\bar{z} + z) \\
 &= x\bar{y} + xyz \\
 &= x(\bar{y} + y) \\
 &= x
 \end{aligned}$$

For  $B$ ,

$$\begin{aligned}
 B &= \bar{x}y\bar{z} + \bar{x}yz + x\bar{y}\bar{z} + x\bar{y}z \\
 &= \bar{z}(x\bar{y} + x\bar{y}) + \bar{z}(\bar{x}y + x\bar{y})
 \end{aligned}$$

$$\begin{aligned}
 &= (\bar{x}\oplus y)(z + \bar{z}) \\
 &= (\bar{x}\oplus y)
 \end{aligned}$$

For  $C$ ,

$$\begin{aligned}
 C &= \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}z + xy\bar{z} \\
 &= \bar{x}(\bar{y}z + y\bar{z}) + x(\bar{y}z + y\bar{z}) \\
 &= (\bar{x} + x)(\bar{y}z + y\bar{z}) \\
 &= (\bar{y}z + y\bar{z}) \\
 &= (y\oplus z)
 \end{aligned}$$

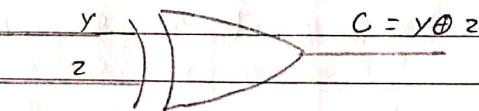
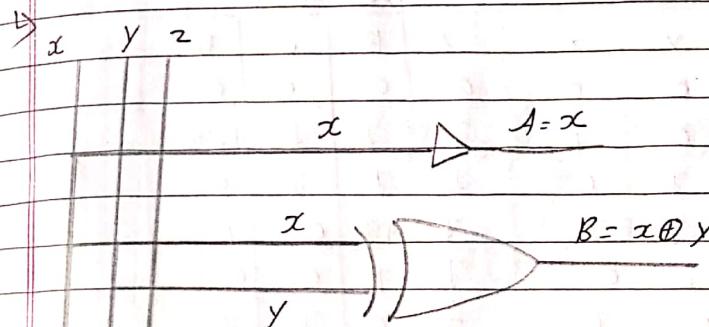


Fig: circuit diagram of 3 bit binary to Gray code converter.

③ # Draw a logical diagram that takes 4 bit binary as an input and provides 2's complement of the input binary number.

- ↳ design of binary to 2's complement converter
- ↳ let inputs  $w, x, y, z_1 = 4$  and outputs be  $A, B, C, D = 4$ .
- ↳ Truth table of binary to 2's complement converter

Inputs				Outputs			
$w$	$x$	$y$	$z_1$	$A$	$B$	$C$	$D$
0	0	0	0	0	0	0	0
0	0	0	1	1	1	1	1
0	0	1	0	1	1	1	0
0	0	1	1	1	1	0	1
0	1	0	0	1	1	0	0
0	1	0	1	1	0	1	1
0	1	1	0	1	0	1	0
0	1	1	1	1	0	0	1
1	0	0	0	1	0	0	0
1	0	0	1	0	1	1	1
1	0	1	0	0	1	1	0
1	0	1	1	0	1	0	1
1	1	0	0	0	1	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	0	1	0
1	1	1	1	0	0	0	1

Boolean expression:

For A,

$\bar{w}\bar{x}$	1	1	1
$\bar{w}x$	1	1	1
$w\bar{x}$	1		
$w\bar{x}$	1		

For B,

$\bar{y}_2 \bar{y}_1 y_2 y_1$	1	1	1
$\bar{w}x$	1		
$wx$	1		
$w\bar{x}$	1	1	1

$$\begin{aligned}
 A &= \bar{w}x + \bar{w}y + \bar{w}z + w\bar{x}\bar{y}\bar{z} \\
 &= \bar{w}(x+y+z) + w(\bar{x}+\bar{y}+\bar{z}) \\
 &= w \oplus (x+y+z)
 \end{aligned}$$

$$\begin{aligned}
 B &= \bar{xy} + \bar{x}_2 + x\bar{y}\bar{z} \\
 &= \bar{x}(y+z) + x(\bar{y}+\bar{z}) \quad \text{using de-moivre law} \\
 &= x \oplus (y+z) \quad \text{i.e. } (\bar{y}+\bar{z})
 \end{aligned}$$

For C,

$\bar{y}_2 \bar{y}_1 y_2 y_1$	1	1
$\bar{w}x$	1	1
$wx$	1	1
$w\bar{x}$	1	1

For D,

$\bar{y}_2 \bar{y}_1 y_2 y_1$	1	1
$\bar{w}x$	1	1
$wx$	1	1
$w\bar{x}$	1	1

$$\begin{aligned}
 C &= \bar{y}_2 + y\bar{z} \\
 &= x \oplus z
 \end{aligned}$$

$$D = z$$

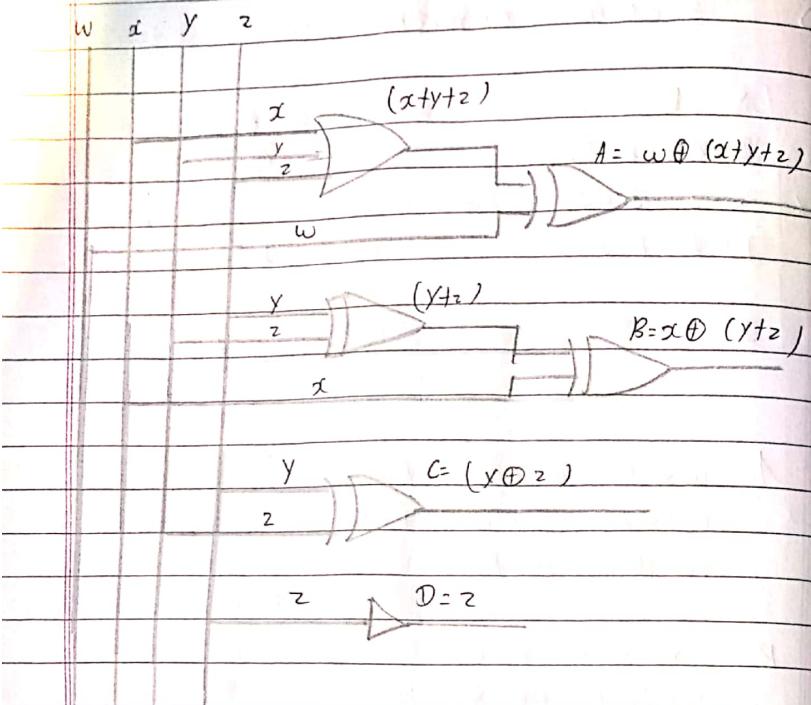


Fig: Circuit diagram of binary to 2's complement converter

## Half Subtractor

design of half subtractor circuit.  
 let input be x and y = 2 and output be d and b where d is difference and b is borrow.

Truth table:

Inputs		Outputs		
x	y	d	b	
0	0	0	0	$D = \bar{A}B + \bar{B}A$
0	1	1	1	
1	0	1	0	$= A \oplus B$
1	1	0	0	

Boolean expression:

$$d = \bar{A}B + A\bar{B}$$

$$= A \oplus B$$

$$b = \bar{x}y$$

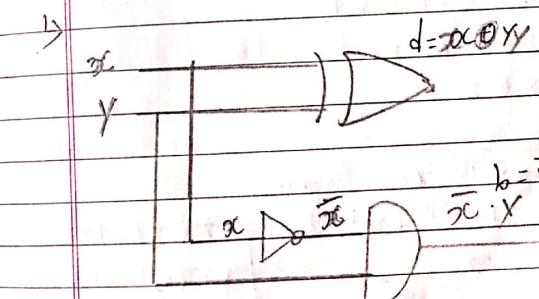


Fig: Circuit diagram of half subtractor

## Full Subtractor

- ↳ design of Full subtractor circuit.
- ↳ let input be  $x, y, z = 3$  and output be  $d$  and  $b$  where  $d$  is difference and  $b$  is borrow.
- ↳ Truth table

Inputs			Outputs	
$x$	$y$	$z$	$d$	$b$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

↳ Boolean expression:

$$\begin{aligned}
 d &= \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xyz \\
 &= \bar{x}(\bar{y}z + y\bar{z}) + x(\bar{y}\bar{z} + yz) \\
 &= \bar{x}(y\oplus z) + x(y\oplus z) \\
 &= \bar{x}(y\oplus z) + x(\overline{y\oplus z}) \\
 &= x \oplus y \oplus z
 \end{aligned}$$

$$\begin{aligned}
 b &= \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}z + xyz \\
 &= \bar{x}(\bar{y}z + y\bar{z}) + yz(\bar{x} + x) \\
 &= \bar{x}(y\oplus z) + yz
 \end{aligned}$$

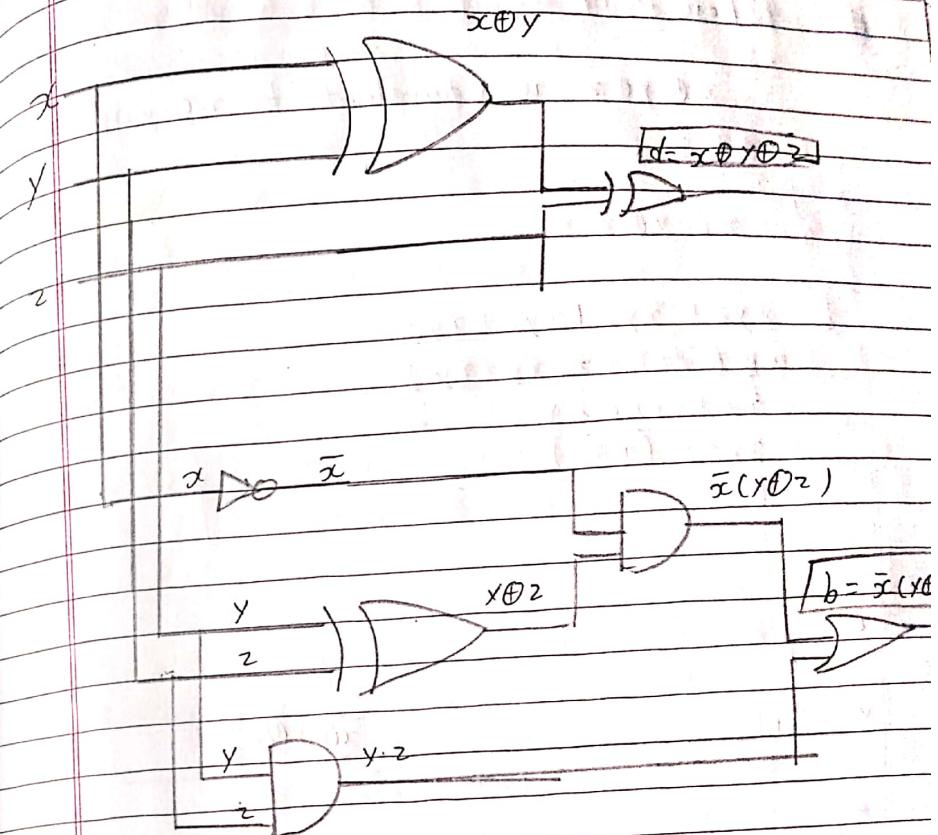


Fig: Circuit diagram of Full subtractor circuit.


From K map,

	$\bar{y}$	$\bar{y}z$	$y\bar{z}$	$yz$
$\bar{x}$	0	1	1	1
$x$	1	1	0	0

$$b = yz + \bar{x}y + \bar{x}z$$

# Implement a full subtractor with two half subtractors and an OR gate.


Half subtractor

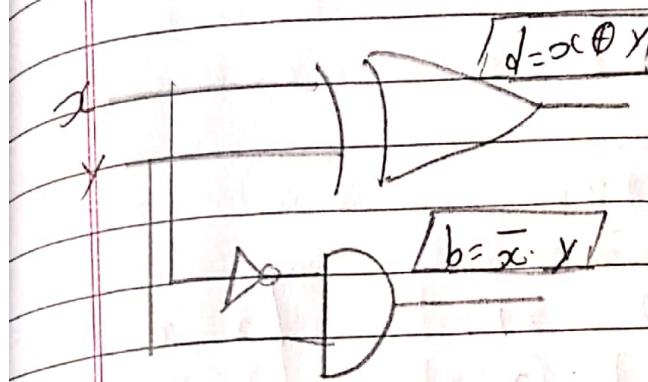

Full subtractor

$$\begin{aligned} d &= x \oplus y \oplus z \\ b &= \bar{x}y + \bar{x}z + yz \\ &= \bar{x}y + z(x \oplus y) \end{aligned}$$

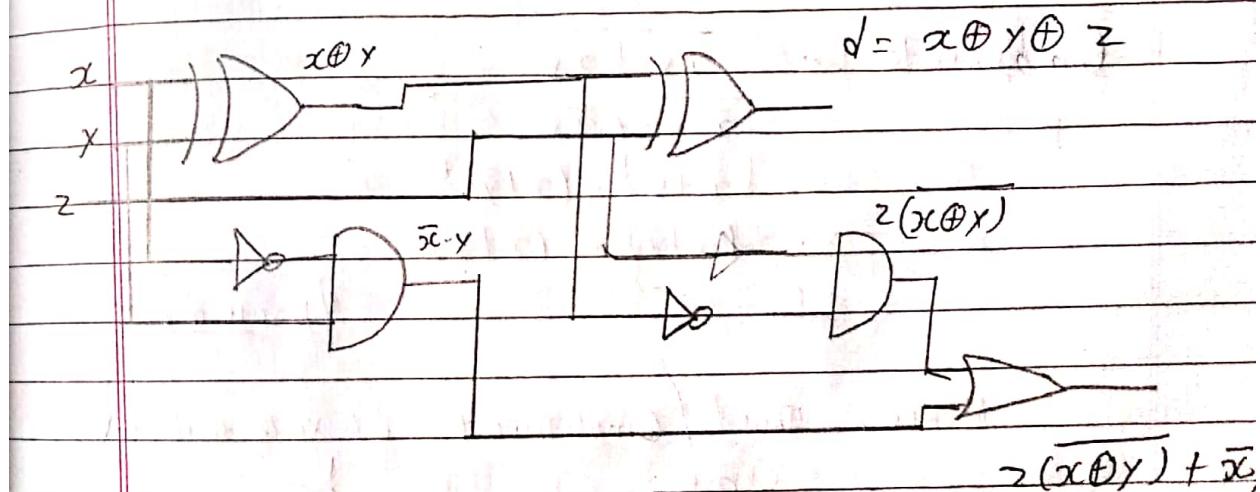Implementing full subtractor with two half subtractors



Show that the dual and complement of  $x \oplus y$  and  $x \otimes y$  are same.

$x \oplus y$

$$\text{Dual: } \bar{x}y + x\bar{y}$$

$$(\bar{x}+y) \cdot (x+\bar{y})$$

Complement:  $\overline{\bar{x}y + x\bar{y}}$

$$= \overline{\bar{x}y} \cdot \overline{x\bar{y}}$$

$$= (\bar{\bar{x}} + \bar{y}) \cdot (\bar{x} + \bar{\bar{y}})$$

$$= (x + \bar{y}) \cdot (\bar{x} + y)$$

$$\left[ \begin{array}{l} \bar{x} = x \\ \bar{y} = y \end{array} \right]$$

$x \otimes y$

$$\text{Dual: } \bar{x}\bar{y} + xy$$

$$(\bar{x}+\bar{y}) \cdot (x+y)$$

$$\text{Complement: } \overline{\bar{x}\bar{y} + xy}$$

$$\overline{\bar{x}\bar{y}} + \overline{xy}$$

$$(\bar{\bar{x}} + \bar{y}) \cdot (\bar{x} + \bar{y})$$

$$(x+y) \cdot (\bar{x}+\bar{y})$$

proved

Hence, Dual & Complement of  $x \otimes y$  and  $x \oplus y$  are same.

Show that  $x \oplus y \otimes z$  is equivalent to  $x \otimes y \oplus z$ .

$$\text{let, } A = x \oplus y$$

$$B = z$$

$x \oplus y \otimes z$

$A \oplus B$

$\bar{A}B + A\bar{B}$

$$\overline{x \oplus y} \cdot z + x \oplus y \cdot \bar{z}$$

$$x \otimes y \cdot z + \overline{x \otimes y} \cdot \bar{z}$$

$$x \otimes y \otimes z \quad \checkmark$$

$$\text{let, } A = x \otimes y$$

$$B = z$$

$x \otimes y \oplus z$

$A \oplus B$

$\bar{A}\bar{B} + A\bar{B}$

$$\overline{x \otimes y} \cdot \bar{z} + x \otimes y \oplus z$$

$$x \otimes y \cdot \bar{z} + \overline{x \otimes y} \cdot z$$

$$x \oplus y \otimes z \quad \checkmark$$

Design a Combinational Circuit which takes a two bit number and generates an output binary number equal to the cube of the input numbers.

design of circuit which takes a two bit number and generates an output binary number equal to cube of input number.

Let input be  $x, y \in \{0, 1\}$  and output be  $A, B = 2^3$ .

Truth table:

Inputs		Outputs				
$x$	$y$	$A$	$B$	$C$	$D$	$E$
0	0	0	0	0	0	0
0	1	0	10	0	0	1
1	0	01	10	0	0	0
1	1	1	1	0	1	1

Logic expression:

$$A = xy$$

$$A = xy$$

$$B = x\bar{y} + \bar{x}y$$

$$= x(\bar{y} + y) = x$$

$$D = xy$$

$$D = xy$$

$$E = \bar{x}y + x\bar{y}$$

$$= y(\bar{x} + x) = y$$

$$= y$$

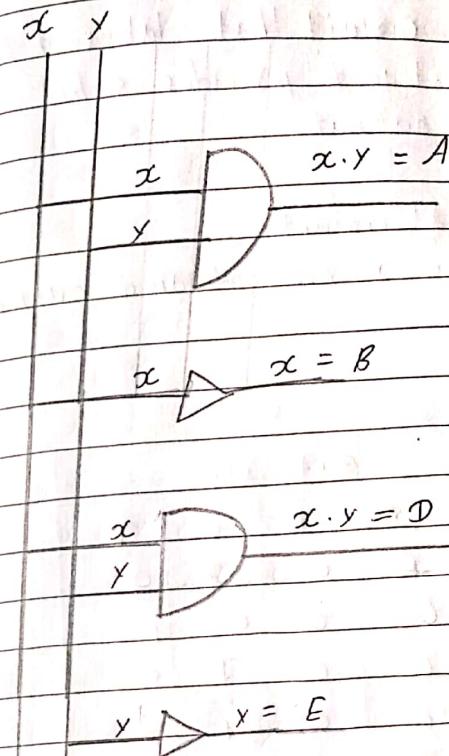


Fig: Circuit diagram of two bit input taking and generating an output binary number equal to the input number

Q Date \_\_\_\_\_  
Page \_\_\_\_\_

Design a logical circuit that takes 4 bit gray code as input and provides 4 bit binary code as an output.

↳ Design of logical circuit - -

↳ let input be  $w, x, y, z = 4$  and output be  $A, B, C, D = 4$ .

↳ Truth table:

Inputs				Outputs			
$w$	$x$	$y$	$z$	$A$	$B$	$C$	$D$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	1
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	1
1	0	0	0	0	1	1	1
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	1	0	1
1	1	1	1	1	1	0	1

Boolean expression

$$A = w\bar{y}\bar{z} + w\bar{x}\bar{y}z + wxyz + wx\bar{y}\bar{z} + w\bar{x}yz$$

$$= w\bar{x}\bar{y}(\bar{z}+z) + wxy(z+\bar{z}) + w\bar{z}y(\bar{z}+z) + w\bar{x}\bar{y}(z+\bar{z})$$

$$= wx(\bar{y}+y) + w\bar{x}(y+\bar{y})$$

$$= wx + w\bar{x}$$

$$= w(x+\bar{x})$$

$$= w$$

For A,

$wx$	$y^2$	$\bar{y}^2$	$\bar{y}z$	$yz$	$y\bar{z}$
$w\bar{x}$					
$\bar{w}x$					
$wx$	1	1	1	1	1
$w\bar{x}$	1	1	1	1	1

For B,

00	01	11	10
00			
01	1	1	1
11			
10	1	1	1

$$A = w$$

$$B = x\bar{w}x + w\bar{x}$$

For C,

00	01	11	10
00	1	1	1
01	1	1	1
11		1	1
10	1	1	1

For D,

00	02	22	20
00	1	1	1
02	1	1	1
22		1	1
20	1	1	1

~~D = Z~~

Ques. w x y z

$$\begin{aligned}
 C &= \bar{w}\bar{x}y + \bar{w}x\bar{y} + wxy + \\ 
 &\quad w\bar{x}\bar{y} \\
 &= \bar{w}(\bar{x}y + x\bar{y}) + w(xy + \bar{x}\bar{y}) \\
 &= \bar{w}(x \oplus y) + w(x \oplus y) \\
 &= \bar{w} \oplus (x \oplus y)
 \end{aligned}$$




$w = A$   
 $x = B$   
 $y = C$   
 $z = D$

$D = A \oplus B \oplus C \oplus D \quad w \oplus x \oplus y \oplus z$

Fig: Circuit diagram

w x y z

$w \rightarrow A = w$

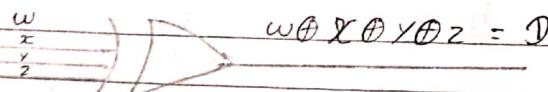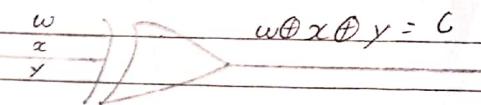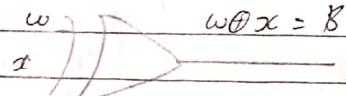

Date \_\_\_\_\_  
Page \_\_\_\_\_  
Patagonia  
Thursday

Design a Combinational Circuit that takes 4 bit binary as input and provides 4 bit gray code as an output.

Design a logical circuit that takes 4 bit binary as input and provides 4 bit gray code as an output.

Let no. of inputs be  $w, x, y, z = 4$  and no. of outputs be  $A, B, C, D = 4$ .

Truth table of logical circuit that takes 4 bit number and provides 4 bit gray code.

Inputs				Outputs			
w	x	y	z	A	B	C	D
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	1	1
1	1	1	1	1	0	0	0

Boolean expression :

For A,

for  $\beta_1$

$wx$	$y^2$	$\bar{y}^2$	$\bar{y}z$	$yz$	$\bar{z}^2$
$w\bar{x}$					
$\bar{w}x$					
$w\bar{x}$	1	1	1	1	1
$w\bar{x}$	1	1	1	1	4

$$A = w$$

$$B = \bar{\omega}x + \omega\bar{x} = \omega \oplus x$$

for C,

For D


$w_1$	$y_2$	$\bar{y}_2$	$\bar{y}_2$	$y_2$	$y_2$
$w\bar{x}$					
$wx$					
$w\bar{x}$					

$$C = \bar{x}y + x\bar{y}$$

$$= x \oplus y$$

$wx$	$y_2$	$\bar{y}_2$	$\bar{y}_2$	$y_2$	$y\bar{2}$
$w\bar{x}$		1	-	1	
$\bar{w}x$		1		1	
$w\bar{x}$		1		1	
$w\bar{x}$		1		1	

$$\mathcal{D} = \hat{y^2} + y_2^-$$

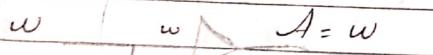

$$B - w \oplus x$$

$$C = x \oplus y$$

$$D = y \theta z$$

Fig: Logical diagram

Design a Combinational Circuit that takes 3 bit number and provides an output binary number equal to the square of the input number.

↳ design a Combinational circuit that takes 3 bit number and provides square of the input number.

Let inputs be  $x, y, z = 3$  and outputs be  $a, b, c$

## Truth table of Combinational Circuit:

Inputs			Outputs					
x	y	z	A	B	C	D	E	F
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0	1
1	0	0	0	1	0	0	0	0
0	1	0	1	1	0	0	0	1
1	0	1	0	0	0	1	0	0
1	1	1	1	0	0	0	0	1

Boolean expression:

$$A = xy\bar{z} + \bar{x}yz = xy(\bar{z} + z) = xy$$

$$\beta = x\bar{v}\bar{z} + x\bar{y}z + xy\bar{z} = x\bar{v}\bar{z} + xz$$

$$c = \bar{x}yz + x\bar{y}z = 2(\bar{x}y + xy) = 2(x\oplus y)$$

$$D = \bar{x}y\bar{z} + x\bar{y}\bar{z} = y\bar{z}(\bar{x}+x) = y\bar{z}$$

$$A = xy$$

$$B = x\bar{y}z + xy\bar{z} + x\bar{y}\bar{z}$$

$$= x(\bar{y}z + y\bar{z}) + x\bar{y}\bar{z}$$

$$= x(y\bar{o}_2) + x\bar{y}\bar{z}$$

$$C = z(x\oplus y)$$

$$D = y\bar{z}$$

$$E = 0$$

$$F = \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xy\bar{z}$$


$$= \bar{x}\bar{y}z(\bar{x} + x) + y\bar{z}(\bar{x} + x)$$

$$= \bar{y}z + y\bar{z}$$


$$= z(\bar{y} + x)$$

$$= z$$

$xy_2$

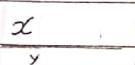


$$A = x \cdot y$$

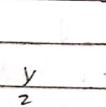


$$B = x(y\bar{o}_2)$$

$$B = x(y\bar{o}_2) + x\bar{y}z$$

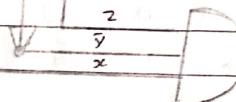

$$(x\oplus y)$$

$$C = (x\oplus y) \cdot z$$

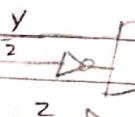

$$D = y\bar{z}$$

$$E = z$$

Fig: Logical diagram

### Gray Code to binary Converter [3-bit]

- design of Combinational Circuit that takes 3 bit number gray Code input and provides 3-bit number output.

Let input be  $x, y, z$  and output be A, B, C.

- Truth table of Combination circuit.

x	y	z	Outputs			write orderly
			A	B	C	
0	0	0	0	0	0	
0	0	1	0	0	1	
0	1	0	0	1	0	
0	1	1	0	1	1	
1	0	0	1	0	0	
1	0	1	1	0	1	
1	1	0	1	1	0	
1	1	1	1	1	1	

- Boolean expression:

$$\begin{aligned} A &= xy\bar{z} + xy\bar{z} + x\bar{y}z + x\bar{y}\bar{z} \\ &= xy(\bar{z} + z) + x\bar{y}(z + \bar{z}) \\ &= xy + x\bar{y} \\ &= x(y + \bar{y}) \\ &= x \end{aligned}$$

$$\begin{aligned}
 B &= \bar{x}yz + \bar{x}y\bar{z} + x\bar{y}z + xy\bar{z} \\
 &= \bar{z}(yz + \bar{y}\bar{z}) + \bar{x}(y\bar{z} + x\bar{y}) \\
 &= \bar{z}(x \oplus z) + \bar{x}(y \oplus z) \\
 &= \bar{z}(y \oplus z) + \bar{x}(x \oplus y)
 \end{aligned}$$

$$\begin{aligned}
 C &= \bar{x}\bar{y}z + \bar{x}y\bar{z} + xy\bar{z} + x\bar{y}\bar{z} \\
 &= \bar{z}(\bar{x}y + x\bar{z}) + \bar{z}(\bar{x}\bar{y} + xy) \\
 &= \bar{z}(x \oplus y) + \bar{z}(x \oplus z) \\
 &= \bar{z}(x \oplus y) + \bar{z}(x \oplus y) \\
 &= z \oplus (x \oplus y)
 \end{aligned}$$

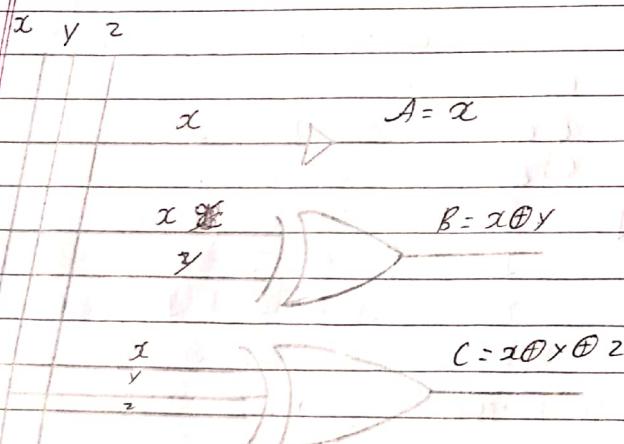


Fig: logical diagram of 3 bit gray code as input and

Date \_\_\_\_\_  
Page \_\_\_\_\_

Date \_\_\_\_\_  
Page \_\_\_\_\_

Design of Parity Generator  
Design of parity checker

Parity generator are of two types:

- ① Odd parity
- ② Even parity

Parity is a mechanism to ensure that transmission is right or not.

It can be checked by odd parity and even parity.

In odd parity, p bit depends upon the number of 1's in input.

In odd parity, if there is even number of 1's in input then we need to add more 1 in p bit. And in even parity if there is odd number of 1's in input then we need to add more 1 in p bit to make it even.

When data is transmitted from one location to another, it is necessary to know at the receiving end whether received data is free of error. A simple form of error detection is achieved by adding an extra bit to the transmitted

## Design of 3 bit odd parity generator.

- ↳ design of 3 bit odd parity generator,
- ↳ let inputs be  $x, y, z$  and output be  $p=1$
- ↳ Truth table of 3 bit odd parity generator.

Inputs	Output		
$x$	$y$	$z$	$p$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

- ↳ Boolean expression from truth table:

$$p = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + x\bar{y}z + xy\bar{z}$$

$$p = \bar{x}(y\oplus z) + x(\bar{y}\oplus z)$$

$$p = \bar{x}\bar{y} \quad \bar{x}(y \oplus z) + x(y \oplus z) \quad \bar{x}(y \oplus z) + x(y \oplus z)$$

$$p = \bar{x}(y \oplus z) \quad x \oplus (y \oplus z)$$

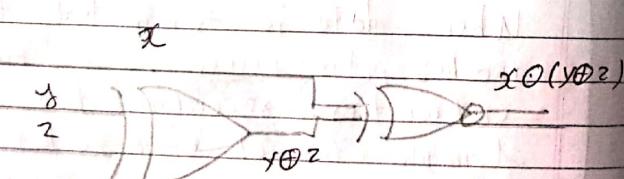


Fig: logical diagram of 3 bit odd parity generator

## Odd parity Checker

- ↳ design of a 3 bit odd parity checker.
- ↳ let inputs be  $x, y, z, p=1$  and outputs

↳ Truth table :

Inputs				Output
$x$	$y$	$z$	$p$	$c$
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

Boolean expression:

$x\bar{y}$	$\bar{x}\bar{y}$	$\bar{x}y$	$x\bar{y}$	$xy$
$z_p$	$\bar{z}_p$	$\bar{z}_p$	$z_p$	$\bar{z}_p$
$\bar{x}\bar{y}$	1	1	1	
$\bar{x}y$		1	1	
$x\bar{y}$			1	
$xy$				1

$$C = \bar{x}\bar{y}\bar{z}_p + \bar{x}\bar{y}z_p + \bar{x}y\bar{z}_p + \bar{x}y z_p + xy\bar{z}_p + \\ xy z_p + x\bar{y}\bar{z}_p + x\bar{y}z_p$$

$$C = \bar{x}\bar{y}(\bar{z}_p + z_p) + \bar{x}y(\bar{z}_p + z_p) + xy(\bar{z}_p + z_p) + \\ x\bar{y}(\bar{z}_p + z_p)$$

$$C = \bar{x}\bar{y}(2\oplus p) + \bar{x}y(2\oplus p) + xy(2\oplus p) + x\bar{y}(2\oplus p)$$

$$\leftarrow C = (\bar{x}\bar{y} + xy)(2\oplus p) + (\bar{x}y + x\bar{y})(2\oplus p)$$

$$C = (x\bar{y}) (2\oplus p) + (\bar{x}\bar{y})(2\oplus p)$$

$$C = (x\bar{y}) (2\oplus p) + (\bar{x}\bar{y})(2\oplus p)$$

$$C = x\bar{y} \oplus z_p$$

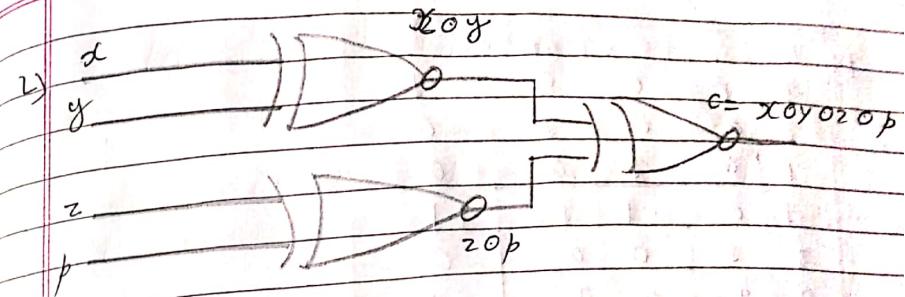


Fig: Logical diagram of odd parity checked.

[H.W]

(70)

Design of 4 bit even parity gen.

- ↳ design of 4 bit even parity generator.
- ↳ let inputs be A, B, C, D and output be P.
- ↳ Total no. of input = 4 and output = 1.

Inputs				Output
A	B	C	D	P
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	0	1	0	0
0	1	1	1	1

1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

↳ Boolean expression:

by using K-Map,

	CD			
AB	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{A}\bar{B}$	1	1	1	
$\bar{A}B$	1	1		
$A\bar{B}$	1	1	1	
$AB$				

$$P = A \oplus B \oplus C \oplus D$$

Odd to gadda kheri

XNOR dko thye values

Even ma XOR Adya

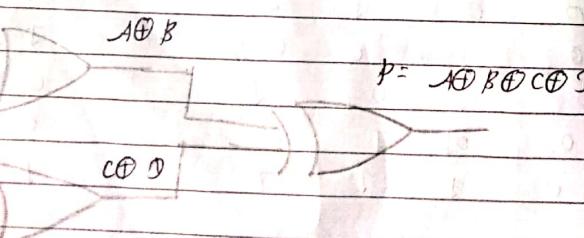


Fig: Logical diagram of 4 bit even parity checker.

## Even Parity Checker

↳ design of 3 bit even polarity checker.

↳ Total no. of input = 4 and output = 1.

↳ Let inputs be  $A, B, C, D$  &  $x, y, z$  & output be  $C$ .

↳ Truth table of 3 bit even polarity checker.

Inputs				Outputs
$x$	$y$	$z$	$p$	$C$
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

↳ Boolean expression:

$x, y$	$\bar{x}, \bar{y}$	$\bar{x} \bar{y}$	$\bar{x} y$	$x \bar{y}$	$x y$	$\bar{x} \bar{y} \bar{p}$	$\bar{x} \bar{y} p$	$\bar{x} y \bar{p}$	$\bar{x} y p$	$x \bar{y} \bar{p}$	$x \bar{y} p$	$x y \bar{p}$	$x y p$
0, 0	1, 1	1	1	1	0	1	0	1	0	1	0	0	0
0, 1	1, 0	0	1	0	1	0	1	0	1	1	0	1	1
1, 0	0, 1	0	0	1	0	0	0	1	0	0	1	0	0
1, 1	0, 0	0	0	0	1	0	0	0	1	0	1	1	1

$$C = \bar{x}\bar{y}\bar{z}\bar{p} + \bar{x}\bar{y}z\bar{p} + \bar{x}x\bar{z}\bar{p} + \bar{x}y\bar{z}p + \\ x\bar{y}\bar{z}\bar{p} + xy\bar{z}\bar{p} + x\bar{y}z\bar{p} + x\bar{y}zp$$

$$C = \bar{z}\bar{p}(\bar{x}\bar{y} + xy) + z\bar{p}(\bar{x}\bar{y} + x\bar{y}) + \bar{z}\bar{p}(\bar{x}\bar{y} + x\bar{y}) + \\ z\bar{p}(\bar{x}\bar{y} + xy)$$

$$C = \bar{z}\bar{p}(x\bar{y}) + z\bar{p}(x\bar{y}) + \bar{z}\bar{p}(x\bar{y}) + z\bar{p}(x\bar{y})$$


$$C = (\bar{z}\bar{p} + z\bar{p})(x\bar{y}) + (z\bar{p} + \bar{z}\bar{p})(x\bar{y})$$

$$C = (z\bar{p})(x\bar{y}) + (\bar{z}\bar{p})(x\bar{y})$$

$$C = \underbrace{(z\bar{p})(\overline{x\bar{y}})}_B + \underbrace{(\bar{z}\bar{p})}_{\bar{A}} + (x\bar{y})_A$$

C =

$$x\bar{y}\oplus z\bar{p}$$

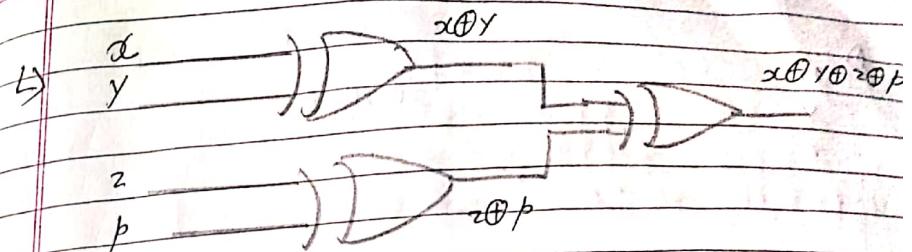

design of 3 bit even parity generator

↳ design of 3 bit even parity generator.  
no. of input = 3 and output = 1.

↳ let input be  $x, y, z$  and output be  $p$ .  
Truth table:

Inputs			Outputs
$x$	$y$	$z$	$p$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

↳ Boolean expression:

$$\bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z} + x\bar{y}\bar{z} + xy\bar{z}$$

$$= z(\bar{x}\bar{y} + x\bar{y}) + \bar{z}(\bar{x}\bar{y} + x\bar{y})$$

$$= z(x\bar{y}) + \bar{z}(x\bar{y})$$

$$= z(x\bar{y}) + \bar{z}(x\bar{y}) \Rightarrow x\bar{y} \oplus z$$

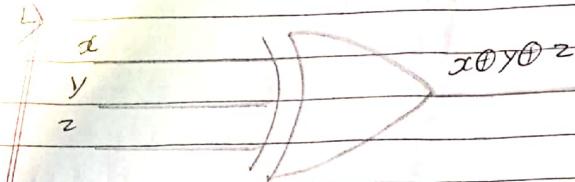


Fig: logical diagram of 3 bit even parity generator

Odd parity:

[3 bit] Odd parity generator -  $x \oplus y \oplus z$

[3 bit] odd parity checker -  $x \otimes y \otimes z \oplus p$

[4 bit] odd parity generator -  $x \otimes y \otimes z \otimes w \oplus p$

Even parity:

[3 bit] Even parity generator =  $x \otimes y \oplus z$

[3 bit] Even parity checker =  $x \otimes y \otimes z \oplus p$

[4 bit] Even parity generator =  $x \otimes y \otimes z \otimes w \oplus p$

Odd

Even

P.G -  $x \otimes y \oplus z$

P.C -  $x \otimes y \otimes z \oplus p$

P.G -  $w \otimes x \otimes y \otimes z$

P.G. -  $x \otimes y \oplus z$

P.C. -  $x \otimes y \otimes z \oplus p$

P.G. -  $x \otimes y \otimes z \otimes w \oplus p$

Date: 15  
Page: Monday  
3<sup>rd</sup> class

Date: \_\_\_\_\_  
Page: \_\_\_\_\_

## Carry Propagation

There are two types of carry:

- ① Input carry [ $c_i$ ]
- ② Output carry [ $c_{i+1}$ ]

$$\text{let } p_i = A_1 \oplus B_1 \\ c_1 = A_1 B_1$$

For full adder circuit,

$$\begin{aligned} \text{Sum } i &= A_1 \oplus B_1 \oplus c_i \\ &= p_i \oplus c_i \end{aligned}$$

$$\begin{aligned} \text{Carry } i+1 &= (A_1 \oplus B_1) c_i + A_1 B_1 \\ &= p_i c_i + G_1 - 0 \end{aligned}$$

$$G_1 = p_0 c_0 + G_0$$

$$\text{when } i=1, G_2 = p_1 c_1 + G_1 = G_1 + p_1 G_0 + p_1 G_0$$

$$\text{when } i=2, G_3 = p_2 c_2 + G_2 = -p_2 (p_1 c_1 + G_1) p_2 (p_1 c_1 + G_1) + G_2 + p_2 G_1 + p_2 p_1 G_0 + p_2 p_1 G_0 p_2$$

$$\begin{aligned} \text{when } i=3, G_4 &= p_3 c_3 + G_3 \\ &= -p_3 (p_2 c_2 + G_2) \end{aligned}$$

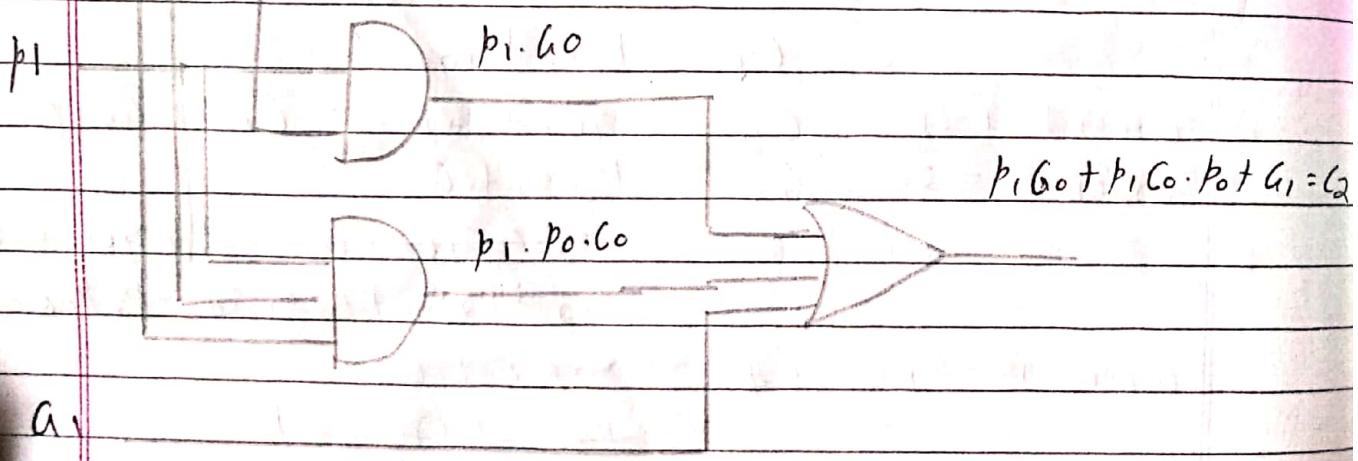
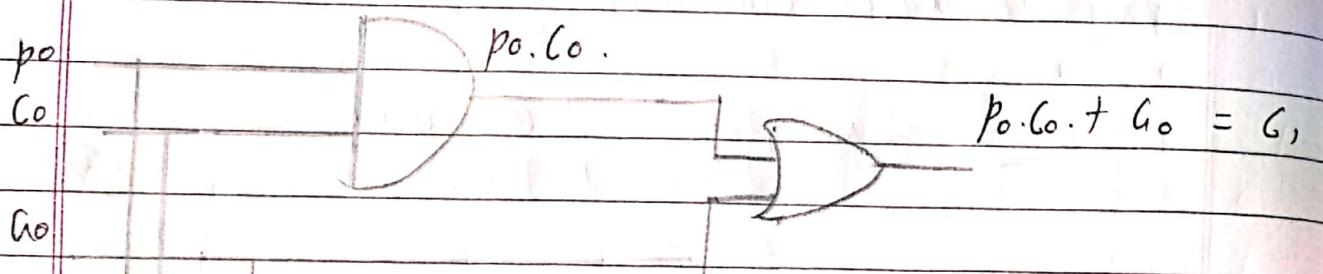
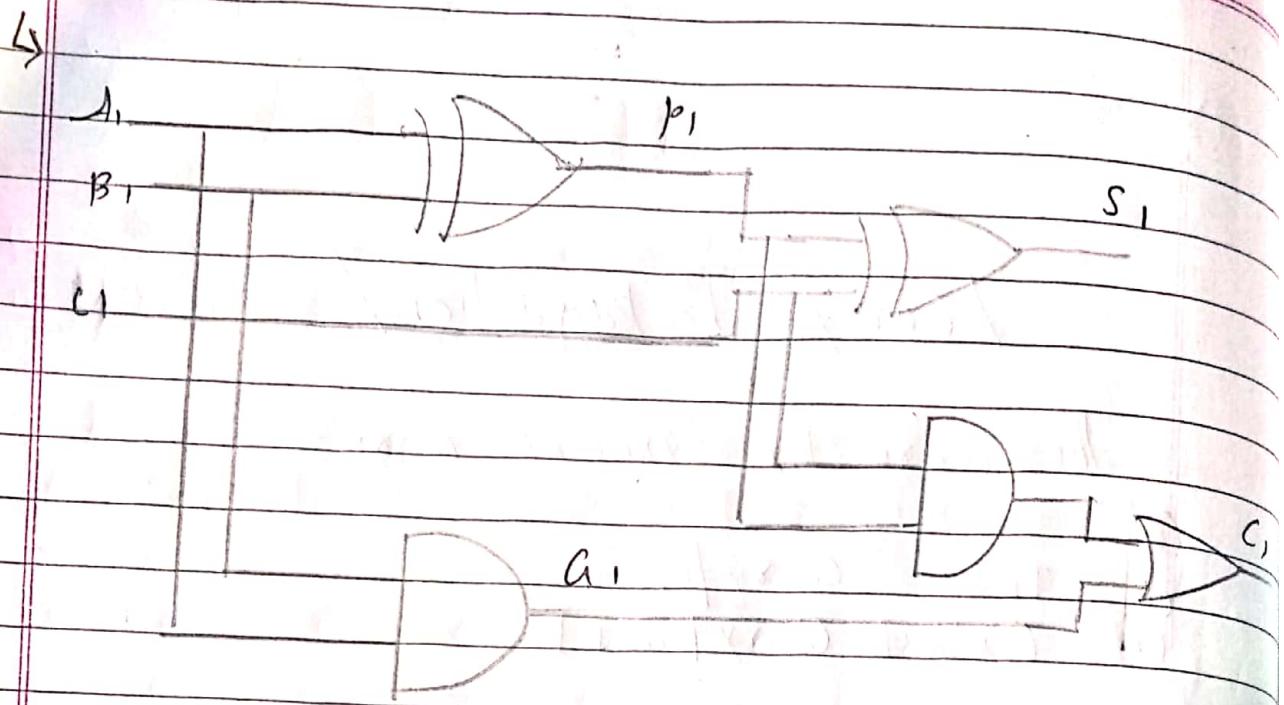


Fig: Logical Diagram

Q1) Design of BCD adder.

## BCD ADDER

↳ Design of BCD Adder,

↳ Truth table:

Decimal	Binary Sum	BCD Sum
K	$Z_8$ $Z_7$ $Z_6$ $Z_5$	C $S_8$ $S_7$ $S_6$ $S_5$
0	0 0 0 0	0 0 0 0 0 0
1	0 0 0 1	0 0 0 0 0 1
2	0 0 1 0	0 0 0 0 1 0
3	0 0 1 1	0 0 0 1 0 0
4	0 1 0 0	0 0 1 0 0 0
5	0 1 0 1	0 0 1 0 1 0
6	0 1 1 0	0 0 1 1 0 0
7	0 1 1 1	0 0 1 1 1 0
8	1 0 0 0	0 1 0 0 0 0
9	1 0 0 1	0 1 0 0 1 0
10	1 0 1 0	0 1 0 1 0 0
11	1 0 1 1	0 1 0 1 1 0
12	1 1 0 0	0 1 1 0 0 0
13	1 1 0 1	0 1 1 0 1 0
14	1 1 1 0	0 1 1 1 0 0
15	1 1 1 1	0 1 1 1 1 0
16	1 0 0 0	1 0 1 0 0 1
17	1 0 0 1	1 0 1 0 1 0
18	1 0 1 0	1 0 1 1 0 0
19	1 0 1 1	1 0 1 1 1 0
20	1 1 0 0	1 1 0 0 0 0
21	1 1 0 1	1 1 0 0 1 0
22	1 1 1 0	1 1 0 1 0 0
23	1 1 1 1	1 1 0 1 1 0
24	0 0 0 0	1 1 1 1 0 0
25	0 0 0 1	1 1 1 1 1 0
26	0 0 1 0	1 1 1 1 1 1
27	0 0 1 1	1 1 1 1 1 1
28	0 1 0 0	1 1 1 1 1 1
29	0 1 0 1	1 1 1 1 1 1
30	0 1 1 0	1 1 1 1 1 1
31	0 1 1 1	1 1 1 1 1 1

Boolean expression:


↳ by using K-map

$\bar{K} \cdot \bar{Z}_8$	$\bar{Z}_8 \cdot \bar{Z}_7$	$\bar{Z}_7 \cdot \bar{Z}_6$	$\bar{Z}_6 \cdot \bar{Z}_5$	$\bar{Z}_5 \cdot \bar{C}$
$\bar{K} \cdot Z_8$	$Z_8 \cdot \bar{Z}_7$	$Z_7 \cdot \bar{Z}_6$	$Z_6 \cdot \bar{Z}_5$	$Z_5 \cdot C$
$K \cdot \bar{Z}_8$	$\bar{Z}_8 \cdot Z_7$	$Z_7 \cdot \bar{Z}_6$	$Z_6 \cdot \bar{Z}_5$	$Z_5 \cdot \bar{C}$
$K \cdot Z_8$	$Z_8 \cdot Z_7$	$Z_7 \cdot Z_6$	$Z_6 \cdot Z_5$	$Z_5 \cdot C$
$\bar{K} \cdot \bar{Z}_8$	$\bar{Z}_8 \cdot \bar{Z}_7$	$\bar{Z}_7 \cdot \bar{Z}_6$	$\bar{Z}_6 \cdot \bar{Z}_5$	$\bar{Z}_5 \cdot \bar{C}$

↳ Boolean expression by using K-map,

$\bar{K} \cdot \bar{Z}_8$	$\bar{Z}_8 \cdot \bar{Z}_7$	$\bar{Z}_7 \cdot \bar{Z}_6$	$\bar{Z}_6 \cdot \bar{Z}_5$	$\bar{Z}_5 \cdot \bar{C}$
$\bar{K} \cdot Z_8$	$Z_8 \cdot \bar{Z}_7$	$Z_7 \cdot \bar{Z}_6$	$Z_6 \cdot \bar{Z}_5$	$Z_5 \cdot C$
$K \cdot \bar{Z}_8$	$\bar{Z}_8 \cdot Z_7$	$Z_7 \cdot \bar{Z}_6$	$Z_6 \cdot \bar{Z}_5$	$Z_5 \cdot \bar{C}$
$K \cdot Z_8$	$Z_8 \cdot Z_7$	$Z_7 \cdot Z_6$	$Z_6 \cdot Z_5$	$Z_5 \cdot C$
$\bar{K} \cdot \bar{Z}_8$	$\bar{Z}_8 \cdot \bar{Z}_7$	$\bar{Z}_7 \cdot \bar{Z}_6$	$\bar{Z}_6 \cdot \bar{Z}_5$	$\bar{Z}_5 \cdot \bar{C}$

$$C = K + Z_8 Z_7 + Z_8 \cdot Z_7$$

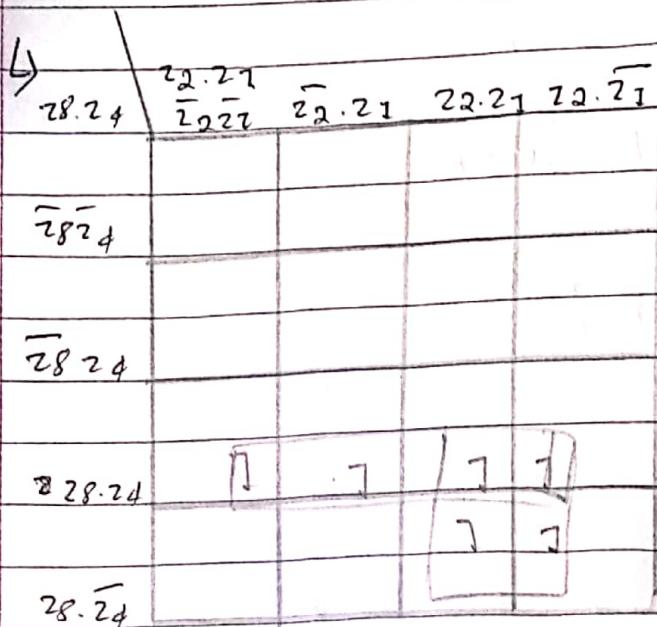

$$C = 28.2_4 + 28.2_2$$

↳

$A_1 A_2 A_3 A_4$        $B_1 B_2 B_3 B_4$

